



American International University Bangladesh (AIUB)
Department of EEE, Faculty of Engineering
Spring 2023-2024
Microprocessor and Embedded Systems (EEE 4103)
Section D, Final Term Quiz 2

Date: 29/04/2024

1. Write a 16-bit control word for the following micro-operations:

- a) $R5 \leftarrow R4 - R2$
- b) $R6 \leftarrow R2 \text{ XOR } R4$
- c) $R6 \leftarrow R1 + R4$

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16
A	B	D	F	C _{in}	H										

) Control word

Binary code	Function of selection variables					
	A	B	D	F with C _{in} = 0	F with C _{in} = 1	H
0 0 0	Input data	Input data	None	$A, C \leftarrow 0$	$A + 1$	No shift
0 0 1	R1	R1	R1	$A + B$	$A + B + 1$	Shift-right, $I_R = 0$
0 1 0	R2	R2	R2	$A - B - 1$	$A - B$	Shift-left, $I_L = 0$
0 1 1	R3	R3	R3	$A - 1$	$A, C \leftarrow 1$	0's to output bus
1 0 0	R4	R4	R4	$A \vee B$	—	—
1 0 1	R5	R5	R5	$A \oplus B$	—	Circulate-right with C
1 1 0	R6	R6	R6	$A \wedge B$	—	Circulate-left with C
1 1 1	R7	R7	R7	\bar{A}	—	—

2. Draw the diagram of a 4-bit status register that has four status bits - carry, sign, zero and overflow flags. Find the four status bits performing the addition operation of the following two numbers of 8-bits :

Number A: (100 + last digit of your middle 5-digit ID number)

Number 2: (120 + last digit of your ID middle 5-digit ID number)